

Jacobs University Bremen

**Natural Science Laboratory
Signals and Systems Lab**

Fall Semester 2021

Lab Theory 2 – RLC Circuits – Frequency Response

Author of the report: Aditya Ojha

Date of execution : 19 October 2021

Prelab: RLC Circuits – Frequency Response

Problem: RLC Resonator

- 1) Show the Bode magnitude plot across the resistor, the capacitor, the inductor, and across both the capacitor and the inductor. Use a 5 V amplitude and vary the frequency starting at 100 Hz up to 100 KHz. Develop a MATLAB script to show all four characteristics in one plot.
 - The voltage calculation across the respective electrical devices was done using the voltage divider principle for the series RLC circuit.

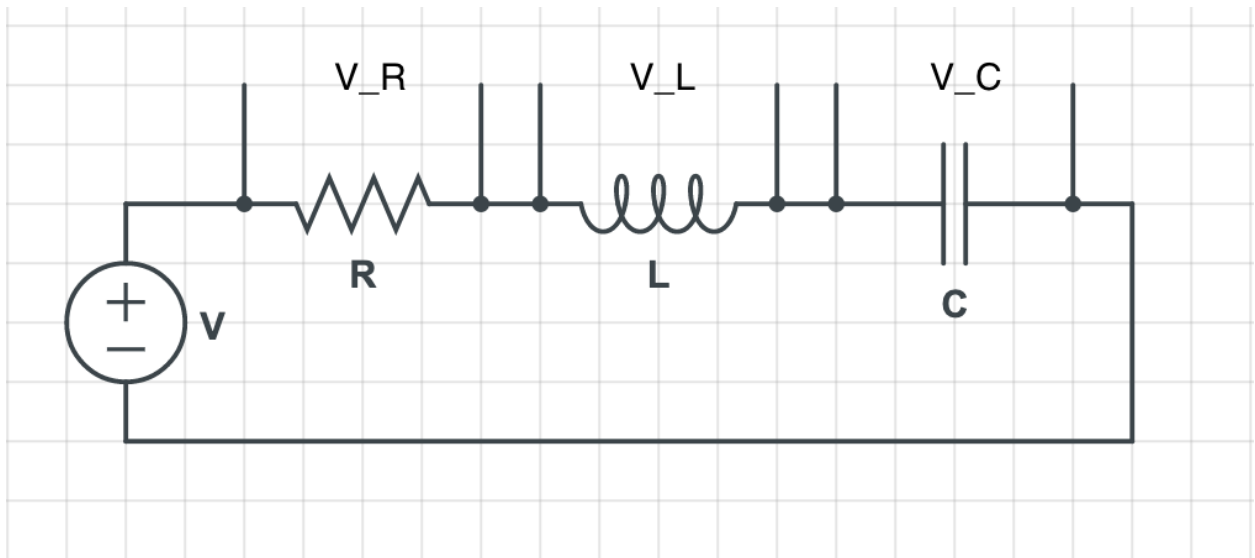


Figure 1: A series RLC circuit

Then the transfer function for each component, $H(j\omega)$ is calculated by the following equation:

$$H(j\omega) = 20 \cdot \log \left(\left| \frac{Z}{Z_{Total}} \right| \right)$$

where,

Z is Impedance of the particular component

Z_{Total} is Total Impedance of the circuit

The values used were: $R = 390\Omega$, $C = 270 \text{ nF}$ and $L = 10 \text{ mH}$.

The plot:

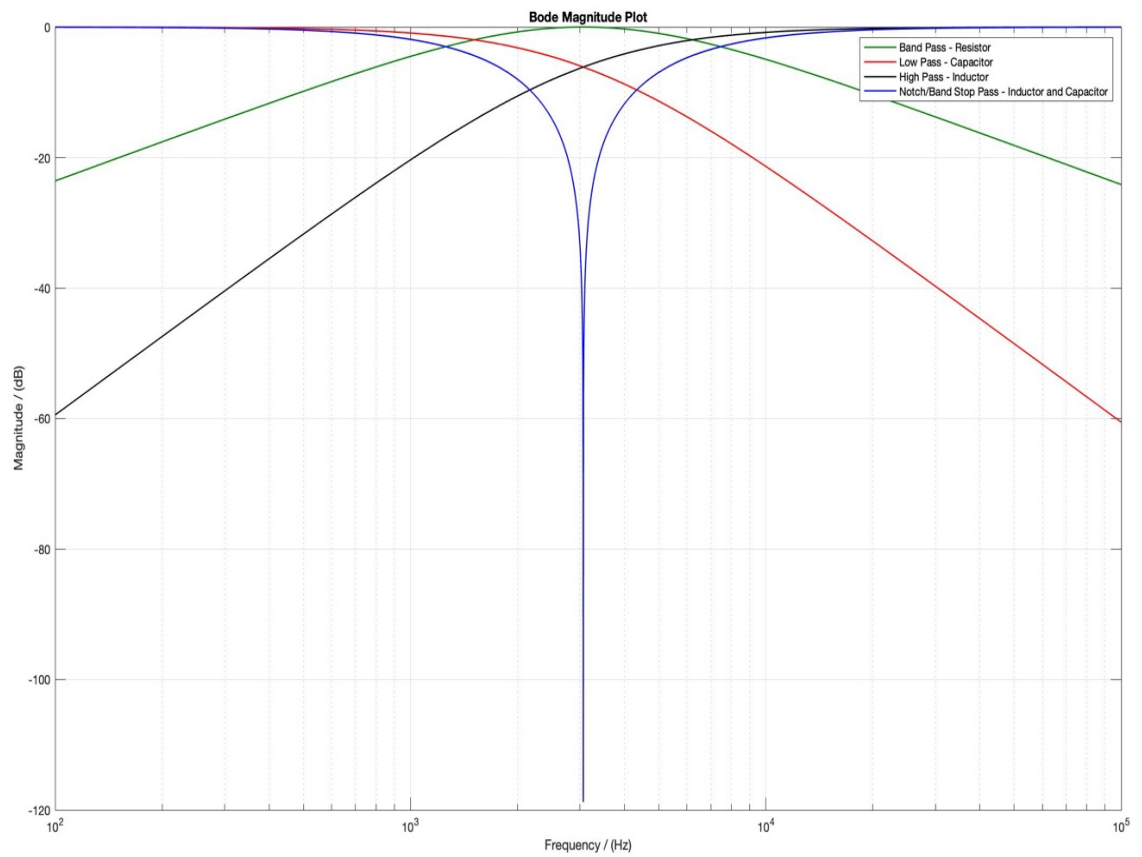


Figure 2: Bode Magnitude Plot for all elements

The MATLAB code used is:

```
%specifying value of the components
R=390;
C=270*10^(-9);
L=10^(-2);
f = logspace(2,5,2000000); %100Hz to 100kHz
omega=2*pi.*f;

Z_R=R; %Impedance across resistor
Z_L=1i*L.*omega; %Impedance across inductor
Z_C=1./(1i*C.*omega); %Impedance across capacitor

Z_T = Z_R+Z_L+Z_C; %Total Impedance

H_R=Z_R./Z_T; % Transfer Function for Resistor
semilogx(f,(20*log10(abs(H_R))), 'color', [0 0.5 0], 'linewidth', 1.1); %
Bode Plot for Resistor
```

```

grid on;
hold on;

H_C = Z_C./Z_T; % Transfer Function for Capacitor
semilogx(f, (20*log10(abs(H_C))), 'r', 'linewidth', 1.1); % Bode Plot for
Capacitor

grid on;
hold on;

H_L= Z_L./Z_T; % Transfer Function for Inductor
semilogx(f, 20*log10(abs(H_L)), 'k', 'linewidth', 1.1); % Bode Plot for
Inductor
grid on;
hold on;

H_L_C = (Z_L+Z_C)./Z_T; % Transfer Function for Inductor and Capacitor
semilogx(f, 20*log10(abs(H_L_C)), 'b', 'linewidth', 1.1); % Bode Plot for
Inductor and Capacitor

title('Bode Magnitude Plot')
xlabel('Frequency / (Hz)')
ylabel('Magnitude / (dB)')
legend('Band Pass - Resistor', 'Low Pass - Capacitor', 'High Pass -
Inductor', 'Notch/Band Stop Pass - Inductor and Capacitor')

```

- 2) Taking the magnitude across the resistance represents a band-pass filter. Extract the bandwidth from the MATLAB plot and calculate the Q-factor.
 - The bode plot for the bandpass filter is plotted. From the plot the cutoff frequency (f_0) and -3 dB frequencies (f_1 and f_2) are found:

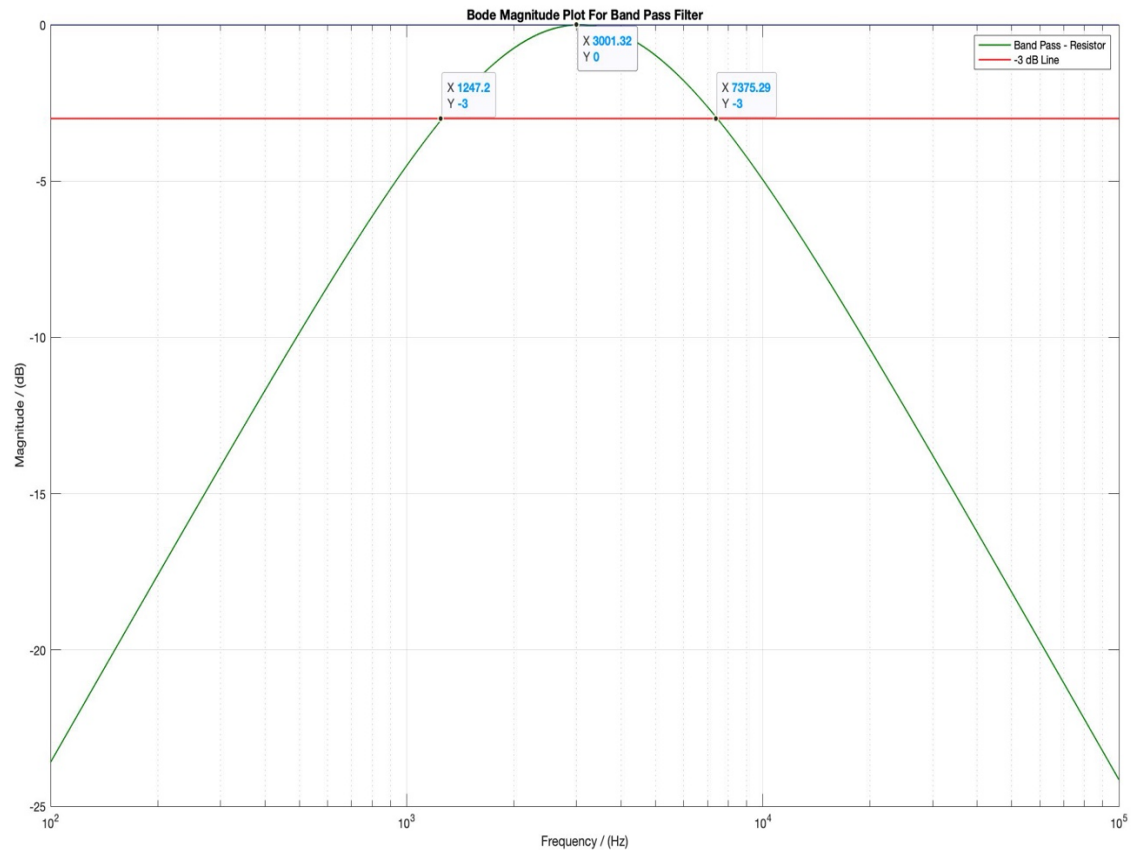


Figure 3: Bode plot of Bandpass Filter

The MATLAB code used is:

```
R=390;
C=270*10^(-9);
L=10^(-2);
f = logspace(2,5,200000);
omega=2*pi.*f;

Z_R=R; %Impedance across resistor
Z_L=1i*L.*omega; %Impedance across inductor
Z_C=1./(1i*C.*omega); %Impedance across capacitor
Z_T = Z_R+Z_L+Z_C; %Total Impedance

H_R=Z_R./Z_T; % Transfer Function for Resistor
semilogx(f,(20*log10(abs(H_R))), 'color', [0 0.5 0], 'linewidth', 1.1); %
Bode Plot for Resistor
```

```

grid on;
hold on;
Con = -3 * (f./f); %-3dB line
[x,y] = intersect(Con, H_R);

semilogx(f,Con,'r', 'linewidth', 1.1);
grid on;
hold on;
Cut = 0*(f./f) ;
[a,b] = intersect(Cut,f);
semilogx(f,Cut,'b');

title('Bode Magnitude Plot For Band Pass Filter');
xlabel('Frequency / (Hz)');
ylabel('Magnitude / (dB)');
legend('Band Pass - Resistor', '-3 dB Line');

```

From the plot:

$$\text{Cutoff frequency } (f_0) = 3001.32 \text{ Hz}$$

-3dB frequencies:

$$f_1 = 1247.20 \text{ Hz}$$

$$f_2 = 7375.29 \text{ Hz}$$

Now,

$$\text{Bandwidth } (B) = f_2 - f_1 = 6128.09 \text{ Hz}$$

$$\text{Quality factor } (Q) = \frac{f_0}{B} = 0.490$$

- 3) Name the remaining filter characteristic measured over the different components, component combinations.

- The filter properties of all the components are:

Electrical Component(s)	Type of Filter
Resistor	Band-Pass
Capacitor	Low Pass
Inductor	High Pass
Capacitor and Inductor	Band-Stop